

PRACTICE EXAM

Difficulty: MEDIUM

Questions: 10

Microelectronic Circuits - Differential Amplifiers Exam

Instructions: Please answer all questions to the best of your ability. Show your work for problem-solving questions to receive partial credit.

Section 1: Multiple Choice Questions (4 points each, 40 points total)

Instructions: Choose the best answer for each question.

Question 1: What is a primary advantage of using differential amplifier configurations in circuit design?

- A) Increased sensitivity to noise
- B) Reduced component count
- C) Reduced sensitivity to noise
- D) Higher power consumption

Question 2: In a perfectly matched MOS differential amplifier with equal common-mode input voltage (V_{CM}) applied to both gates, how is the current I typically divided between the two transistors (Q_1 and Q_2)?

- A) All current flows through Q_1 .
- B) All current flows through Q_2 .
- C) The current is divided equally: $I_{Q1} = I_{Q2} = I/2$
- D) The current division is unpredictable.

Question 3: The differential voltage gain (A_d) of a MOS differential amplifier is given by which formula (neglecting r_o)?

- A) $A_d = 1 / (g_m \cdot R_D)$
- B) $A_d = g_m / R_D$
- C) $A_d = g_m \cdot R_D$
- D) $A_d = R_D / g_m$

Question 4: What is a key reason why differential amplifiers are well-suited for IC (Integrated Circuit) applications?

- A) They require fewer components than other amplifier types.
- B) IC fabrication allows for highly matched devices, and their parameters track well together across changes in temperature and voltage
- C) They have inherently low power consumption.
- D) They are less sensitive to variations in component values.

Section 2: Short Answer Questions (6 points each, 30 points total)

Instructions: Answer each question in 2-3 sentences.

Question 5: Explain why the input stage of an operational amplifier (Op Amp) is often a differential amplifier.

Question 6: Describe the condition in which the MOSFETs in a differential amplifier should operate for proper amplification.

Question 7: In the context of MOS differential amplifiers, what does the term "common-mode voltage (VCM)" refer to, and how is it applied?

Section 3: Problem-Solving Questions (10 points each, 30 points total)

Instructions: Show all work for full credit.

Question 8: A MOS differential amplifier has a differential voltage gain (A_d) of 25 and a drain resistance (R_D) of $5\text{ k}\Omega$. Calculate the transconductance (g_m) of the transistors. (Assume r_o is negligible).

Question 9: In a MOS differential amplifier with a current source I , if $I = 200\text{ }\mu\text{A}$, and the transistors Q_1 and Q_2 are perfectly matched, what are the drain currents (i_{D1} and i_{D2}) of each transistor?

Question 10: Briefly explain how the common-mode voltage affects the bias of the differential amplifier circuit. How can we change the common-mode voltage?