

Find:

$$\beta_1 = \beta_2 = \beta_3 = \beta$$

$$R_o = R_g \parallel \frac{(r_{\pi 3} + R_7)}{(\beta + 1)}$$

$$R_{i3} = r_{\pi 3} + (R_g \parallel R_8)(\beta + 1)$$

$$\beta_3 = \left\{ \begin{array}{l} g_m \\ r_{\pi 3} \\ r_{e3} \end{array} \right.$$

$$R_{i2} = r_{\pi 2} + R_6(\beta + 1)$$

$$\beta_2 = \left\{ \begin{array}{l} g_m \\ r_{\pi 2} \\ r_{e2} \end{array} \right.$$

$$R_{i1}' = r_{\pi 1} + (R_4 \parallel R_5)(\beta + 1)$$


$$R_i = R_1 \parallel R_2 \parallel R_{i1}'$$

$$\beta_1 = \left\{ \begin{array}{l} g_m \\ r_{\pi 1} \\ r_{e1} \end{array} \right.$$

Volt. Gain for α_3

$$A_{v3} = \frac{V_o}{V_2} = \frac{R_8}{r_{e3} + R_B}$$

$$\approx \frac{g_m R_8}{1 + g_m R_8}$$

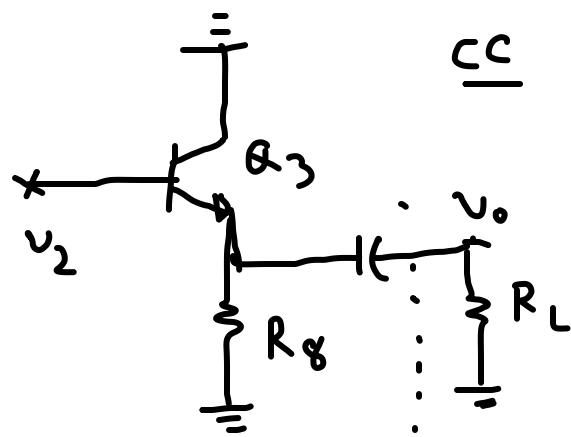


$$r_{e3} = \frac{\alpha}{g_m \beta}$$


Voltage gain for α_2

$$A_{v2} = -\frac{g_m (R_7 || R_{i3})}{1 + g_m R_6}$$

$$= \frac{V_2}{V_1}$$

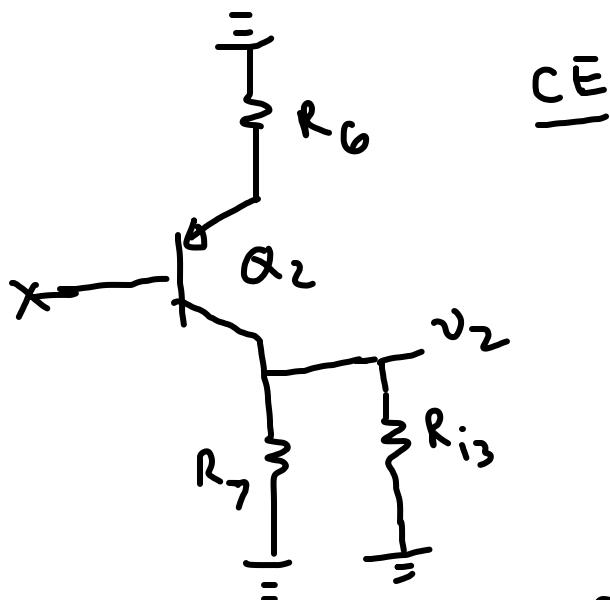


Voltage gain for α_1

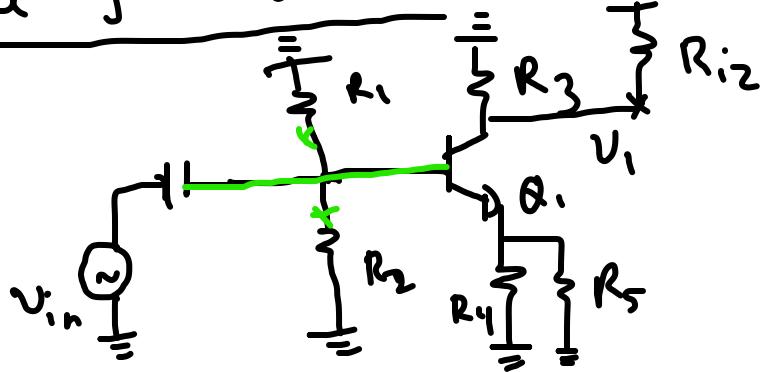

$$A_{vCE} = -\frac{g_m R_C}{1 + g_m R_E}$$

(CE)

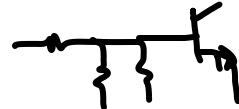

$$A_{v1} = - \frac{g_{m1} (R_3 \parallel R_{i2})}{1 + g_{m1} (R_g \parallel R_S)} = \frac{v_1}{v_{in}}$$

$$\begin{aligned} A_{vo} &= A_{v1} \times A_{v2} \times A_{v3} \\ &= \frac{v_1}{v_{in}} \times \frac{v_2}{v_1} \times \frac{v_o}{v_2} = \frac{v_o}{v_{in}} \end{aligned}$$

$$= () () ()$$

with load

$$A_v = \underline{A_{vo} \times \frac{R_L}{R_L + R_O}}$$

with load

$$A_{v3-L} = \frac{R_g \parallel R_L}{r_{e3} + R_g \parallel R_L}$$

$$A_v = A_{v1} \times A_{v2} \times A_{v3-L}$$

$$g_m = 40 I_C \quad (\text{DC analysis})$$


$$r_k = \frac{B}{g_m}$$

$$r_e = \frac{\alpha}{g_m} = \frac{r_\pi}{B+1}$$

Q₂

10^V
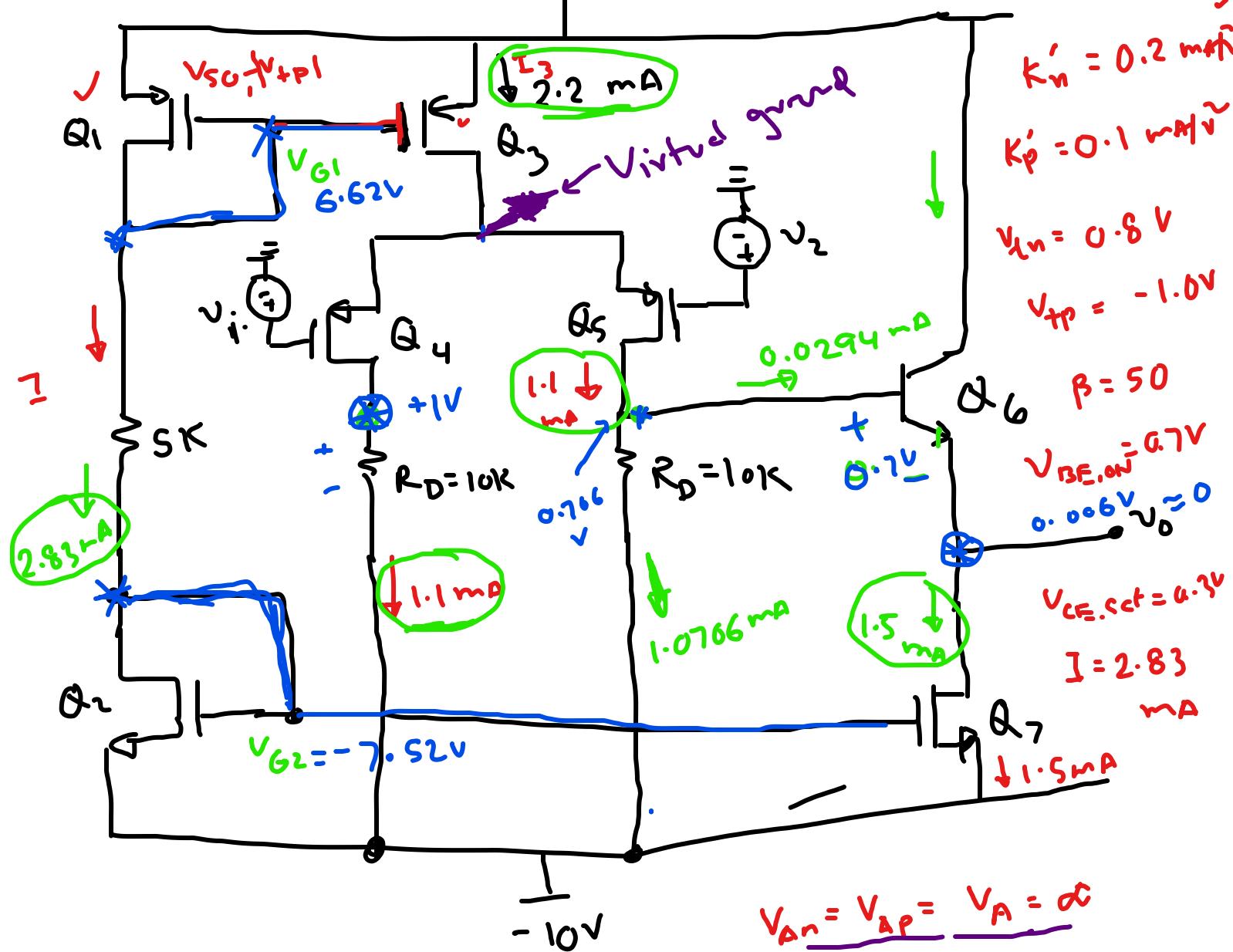
$$\left(\frac{w}{l}\right)_{1,2,4,5} = 10$$



① Find the V_{ov} (overdrive voltage)

$$V_{out} = \sqrt{\frac{2J}{k'_p \times \left(\frac{W}{L}\right)_1}} = \sqrt{\frac{2 \times 2.83}{0.1 \times 10}} = 2.38 V = V_{out}$$

$$V_{ov2} = V_{ov7} = \sqrt{\frac{2I}{K_n' \times \left(\frac{w}{l}\right)_2}} = \sqrt{\frac{2 \times 2.83}{0.2 \times 10}} = 1.68 \text{ V}$$

$$V_{oV4} = V_{oV5} = \sqrt{\frac{2 \times 1.1}{0.1 \times 10}} = 1.48 \text{ V}$$

$$I_{D3} = \frac{1}{2} K_p' \left(\frac{W}{L}\right)_3 V_{ov3}^2$$

$$\frac{I_3}{I_{ref}} = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_{ref}}$$

① Find $\left(\frac{W}{L}\right)_3$ and $\left(\frac{W}{L}\right)_7$

$$\left(\frac{W}{L}\right)_3 = \frac{I_3}{I_{ref}} \times \left(\frac{W}{L}\right)_1 = \frac{2.2}{2.87} \times 10 = 7.77$$

$$\left(\frac{W}{L}\right)_7 = \frac{I_7}{I_{ref}} \times \underbrace{\left(\frac{W}{L}\right)}_{\theta_2 \text{ ref}} = \frac{1.5}{2.83} \times 10 = 5.31$$

② Find the branch current and node voltage

$$I_{B.6} = \frac{1.5}{50+1} = 0.0294 \text{ mA}$$

$$I_{C.6} = I_{B.6} \times 50 = 1.47 \text{ mA}$$

$$V_{SG1} - |V_{tp}| = V_{ov1}$$

$$V_{SG1} = 2.38 + 1 = 3.38 \text{ V}$$

$$V_{S1} - V_{G1} = 3.38 \text{ V} \quad V_A = 10 - 3.38 = 6.62 \text{ V}$$

$$V_{GS2} - V_{thn} = V_{ov2}$$

$$\begin{aligned} V_{G2} &= V_{S2} + V_{thn} + V_{ov2} \\ &= -10 + 0.8 + 1.68 = -7.52 \text{ V} \end{aligned}$$

(c) Common mode input voltage range

Q_3 at margin to find $V_{cm\ max}$

$$\Rightarrow V_{SD3} = V_{ov3}$$

$$10 - V_{D3} = 2.38$$

$$V_{D3} = 10 - 2.38 = 7.62 \text{ V}$$

$$V_{SG4} - |V_{tp}| = V_{ov4}$$



$$V_{S4} - V_{G4} - (V_{tp}) = 1.48$$

$$7.62 - V_{G4} - 1 = 1.48$$

$$V_{G4} = 7.62 - 1 - 1.48$$

$$\approx 5.14$$

$$V_{cm\ max} \leq 5.14 \text{ V}$$

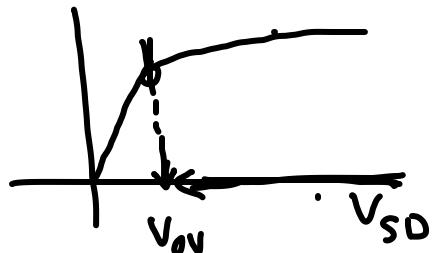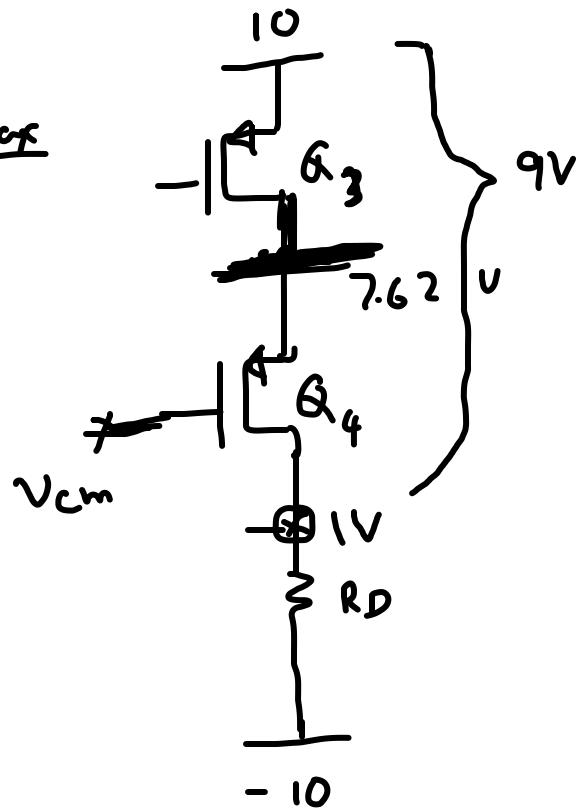

$$\underline{V_{cm} - \text{min}}$$

Q_4 at margin

$$V_{SD4} = V_{ov4}$$

$$V_{S4} - V_{D4} = 1.48$$

$$V_{S4} = 2.48 \text{ V}$$

$$\approx V_{SO4} - |V_{tp}| = V_{ov4}$$



$$V_{S4} - V_{G4} - |V_{tp}| = V_{ov4}$$

$$V_{G4} = V_{S4} - |V_{tp}| - V_{ov4}$$


$$= 2.48 - 1 - 1.48 = 0$$

$$V_{cm \text{ min}} = 0 \text{ V}$$

$$0 \leq V_{cm} \leq 5.14 \text{ V}$$

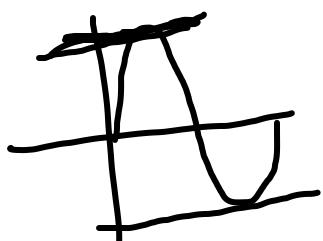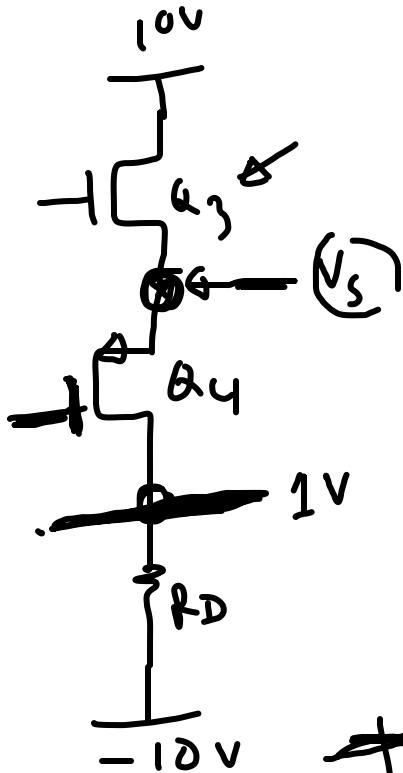

(d) Differential mode gain

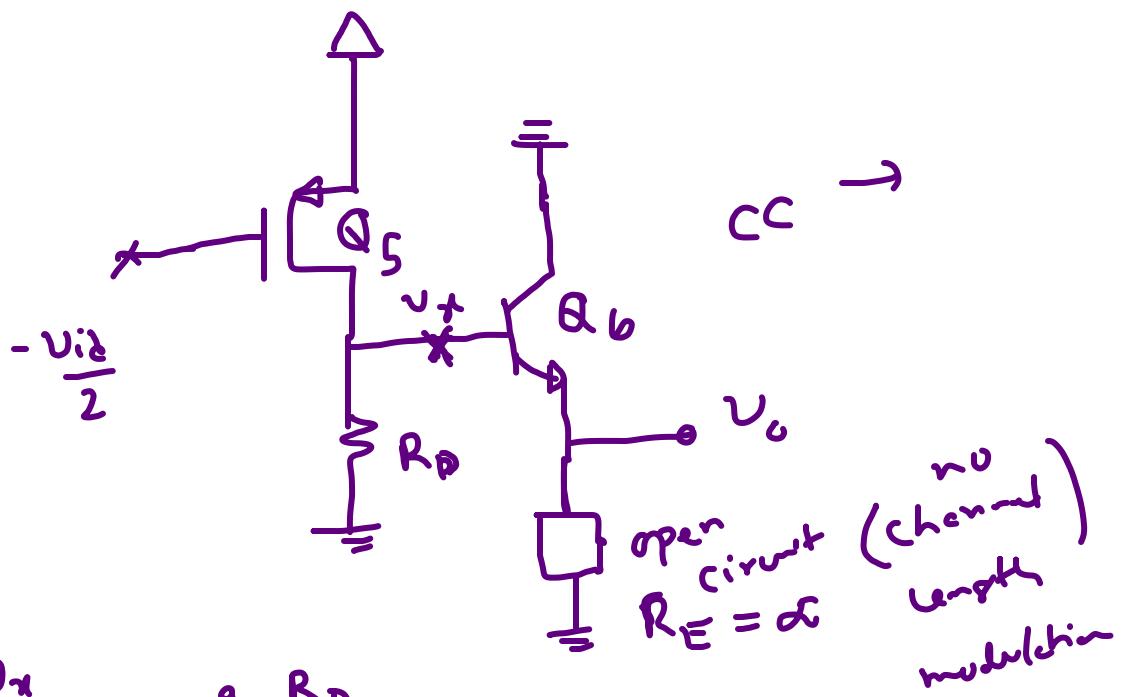

$$\frac{v_x}{-\frac{V_{i_d}}{2}} = -g_{ms} R_D$$

$$-\frac{V_{i_d}}{2}$$

$$\frac{v_x}{v_{in}} = \frac{1}{2} g_{ms} R_D$$

$$\frac{v_o}{v_x} \approx \text{unit } \gamma$$

$$= \frac{g_{mr} R_E}{1 + g_{mr} R_E} \approx 1$$

$$A_{v,d} = \frac{v_o}{v_x} \cdot \frac{v_x}{v_{in}} = \frac{1}{2} g_{ms} R_D$$

$$g_{ms} = \frac{2I_{DS}}{V_{ovs}} = \frac{2 \times 1.1}{1.48} = 1.48 \text{ mS}$$

$$A_{v,d} = \frac{1}{2} \times 1.48 \times 10 = 7.48 \text{ V/V}$$

(d) Repeat part (c) if $V_{An} = 40V$
 $V_{pp} = -20V$
 $V_A = 80V$

$$r_{o5} = \frac{20}{1.1} = \frac{|V_{Apl}|}{I_{DS}}$$



$$= 18.18 \text{ k}\Omega$$

$$r_{o6} = \frac{V_A}{I_C} = \frac{80}{1.47} = 54.42 \text{ k}\Omega$$

$$r_{\pi 6} = \frac{\beta}{g_m b}$$

$$g_m b = 40 \text{ S/C} \times 10^{-12} = 40 \times 10^{-12}$$
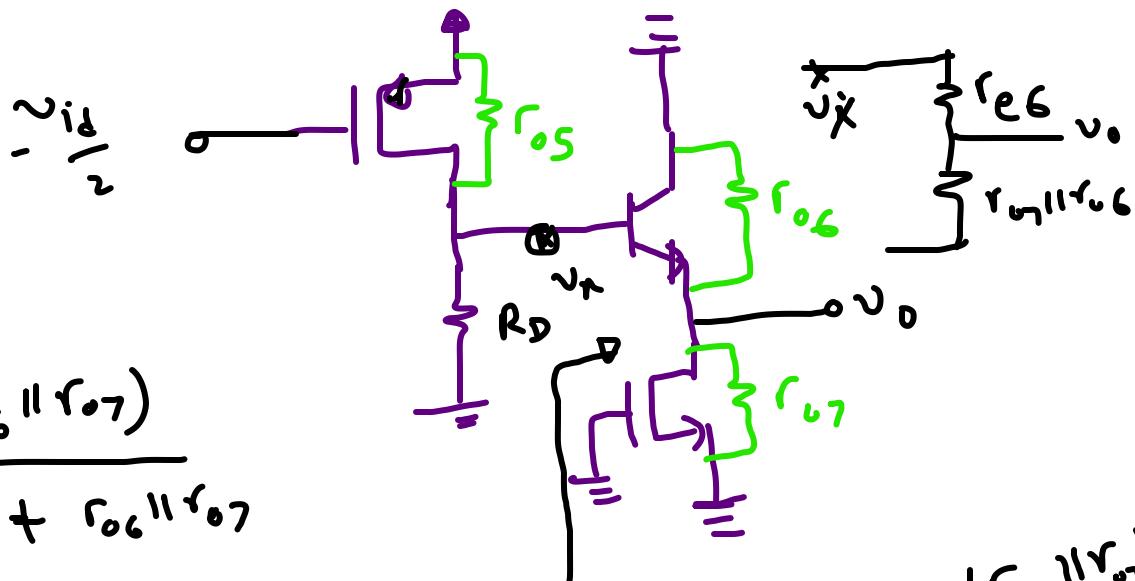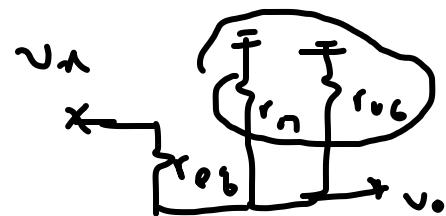
$$r_{o7} = \frac{40}{1.5} = 26.67 \text{ k}\Omega$$



$$\frac{V_o}{V_n} = \frac{(r_{o6} \parallel r_{o7})}{r_{o6} + r_{o6} \parallel r_{o7}}$$

$$r_{e6} = \frac{r_{\pi 6}}{\beta + 1}$$

$$R_i' = r_{\pi 6} + (\beta + 1) (r_{o6} \parallel r_{o7})$$

$$\frac{V_n}{-\frac{V_id}{2}} = -g_m b (R_D \parallel R_i')$$


$$\frac{V_o}{V_n} = \frac{g_m b (r_{o6} \parallel r_{o7})}{1 + g_m b (r_{o6} \parallel r_{o7})} \approx 1$$

$\text{CC} \rightarrow \text{gain unity}$

$$\frac{V_n}{V_{id}} = \frac{1}{2} g_{ms} (R_o \parallel R_i')$$

$$A_v = \frac{V_n}{V_{id}} \cdot \frac{V_o}{V_n} = \frac{V_o}{V_{id}}$$
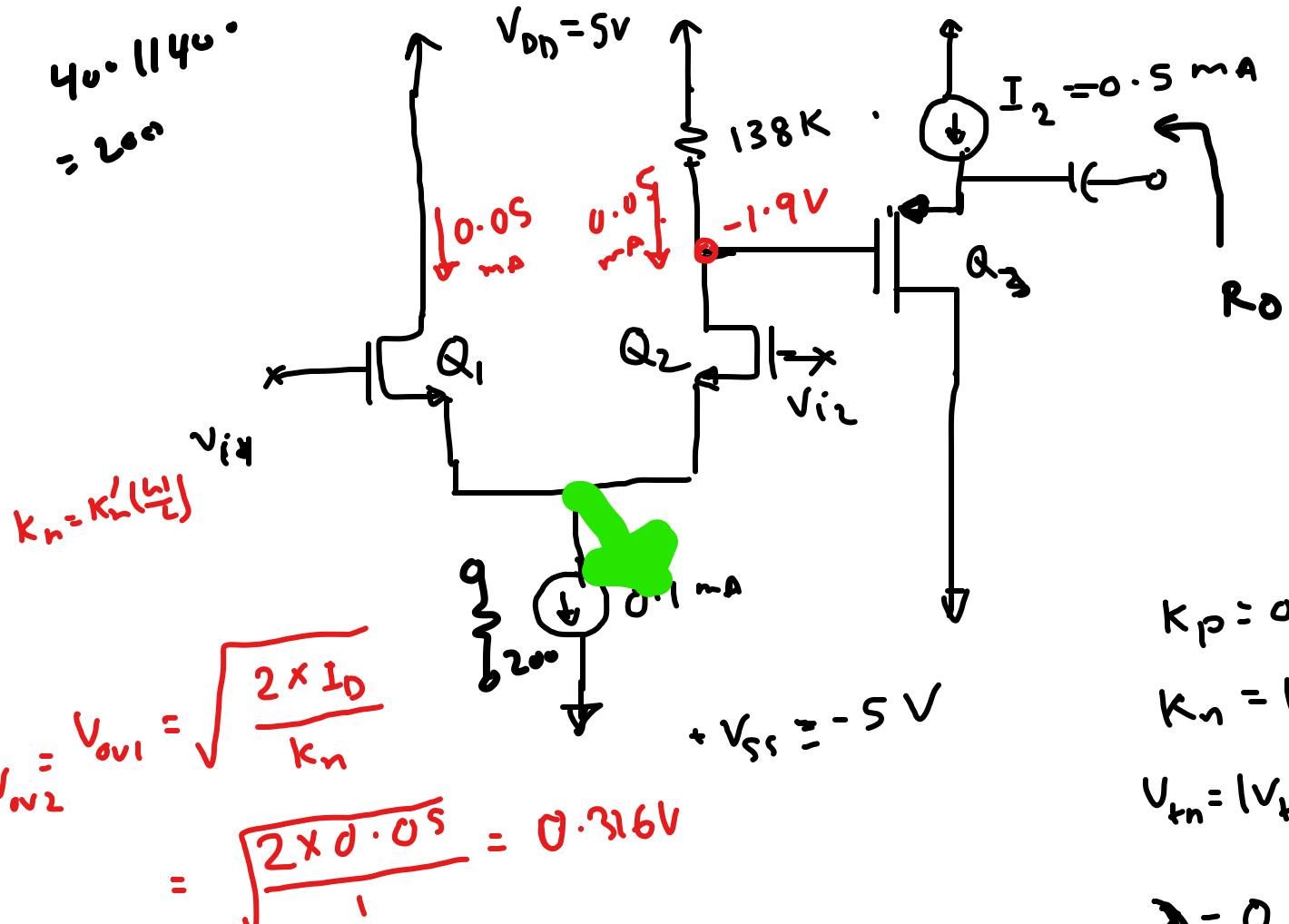
$$= \frac{1}{2} g_{ms} (R_o \parallel R_i') \underbrace{\left(\frac{r_{oc} \parallel r_{o7}}{r_{e6} + r_{oc} \parallel r_{o7}} \right)}$$



$$V_{n2} = V_{ovl} = \sqrt{\frac{2 \times I_D}{k_n}}$$

$$= \sqrt{\frac{2 \times 0.05}{1}} = 0.316V$$

$$V_{o3} = \sqrt{\frac{2 \times 0.5}{0.39}} = 1.661 \text{ V}$$

minimum voltage for the current source = 0.35 V

(a) Common mode voltage gain

Maximum Vcm


Q_2 will operate at margin

$$v_{DS2} = v_{ov2} = 0.316V$$

$$V_{PS} - V_{S2} = 0.316$$

$$V_{S2} = V_{DS} - 0.316$$

$$= -1.9 - 0.316 = -2.216 \text{ V}$$

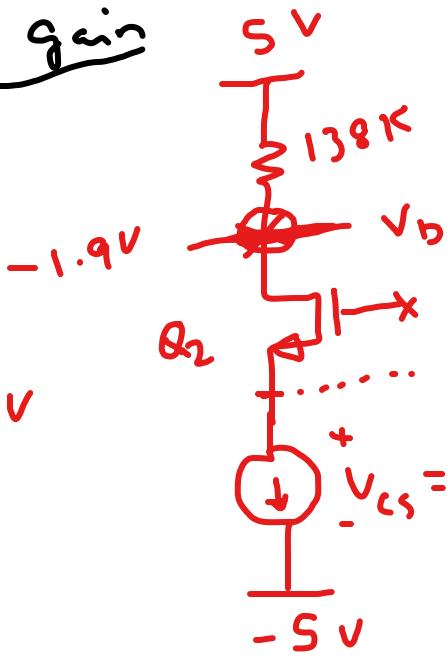

$$V_{GS2} - V_{tn} = V_{ov2}$$

$$V_{G2} - V_{S2} - V_{tn} = V_{ov2}$$

$$V_{G2} = V_{S2} + V_{tn} + V_{ov2} = -2.216 + 0.7 + 0.316$$

$$V_{G2} = V_{S2} + V_{tn} + V_{ov2} = -1.6 \text{ V}$$


Minimum V_{cm}

$$V_{S2} = -5 + 0.35 = -4.65 \text{ V}$$

$$V_{G2} = V_{S2} + V_{tn} + V_{ov2} = -4.65 + 0.3 + 0.316 = -4.034 \text{ V}$$

$$V_{cm-min} = -4.034 < V_{cm} < -1.6 \text{ V}$$

Differential mode voltage gain

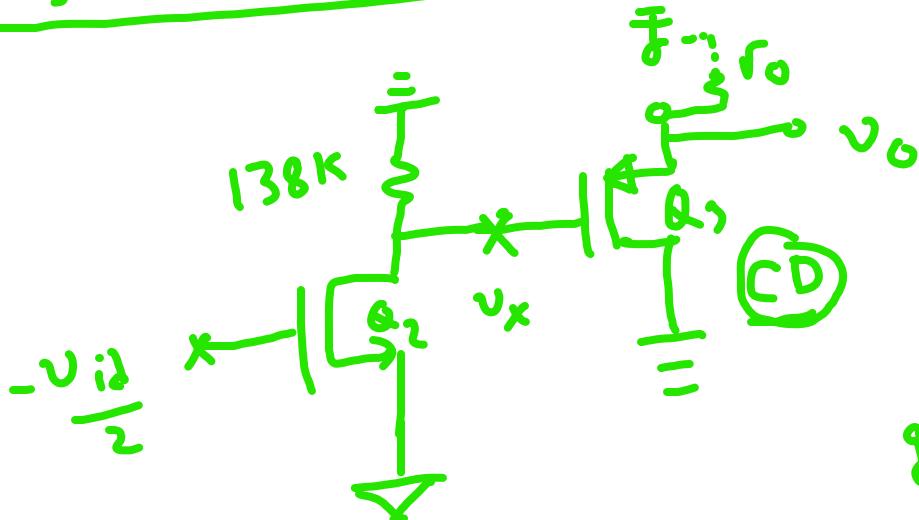

$$g_{m2} = \frac{2I_D}{V_{ov2}}$$

$$\frac{v_n}{-\frac{v_{id}}{2}} = - g_{m2} R_D$$

$$= \frac{2 \times 0.05}{0.316} = 0.3165 \text{ ms}$$

$$\frac{v_n}{v_{id}} = \frac{1}{2} g_{m2} (138) : 21.87 \text{ V/V}$$

$$\frac{v_o}{v_n} \approx 1 = \frac{g_{m3} r_o}{1 + g_{m3} r_o} \quad r_o \rightarrow \infty$$


If r_o is known (e.g. non-ideal current source) $r_o = 20K$

$$A_{v, d} = \left(\frac{g_{m3} r_o}{1 + g_{m3} r_o} \right) \left(\frac{1}{2} g_{m2} R_D \right) = \frac{0.92588}{\times 21.87} \text{ V/V}$$

$$= 20.22 \text{ V/V}$$



Common mode voltage gain

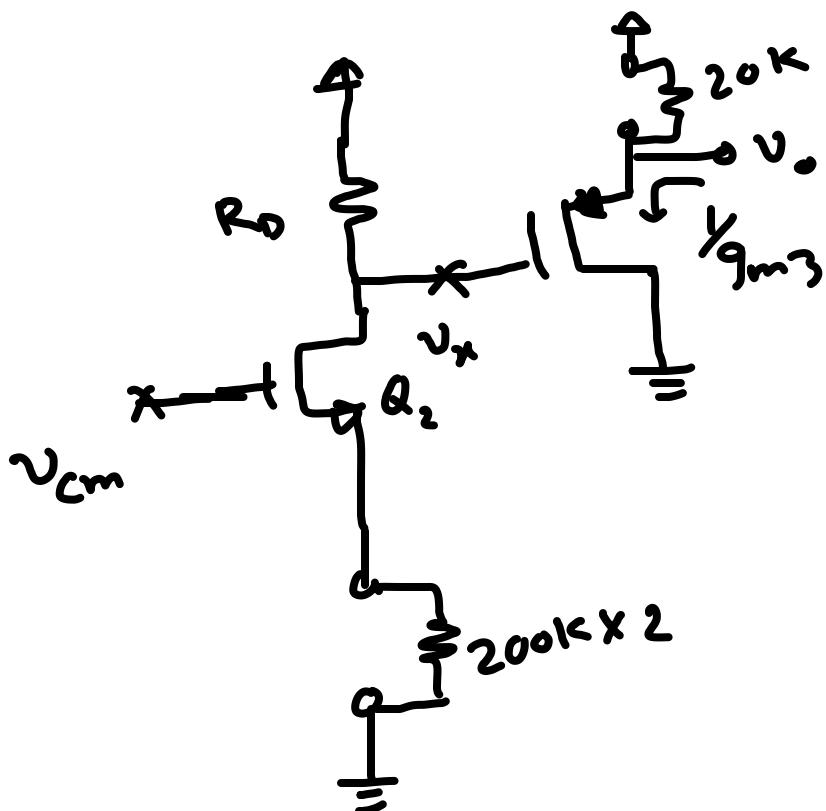

we must
need
the internal
resistance
of the
current
source

$$\frac{v_x}{v_{cm}} = \frac{g_{m2} R_D}{1 + g_{m2}(2 \times 200)} = -0.679 \text{ V/V}$$

$$\frac{v_o}{v_n} = \frac{20}{20 + \frac{1}{g_m}} = 0.92587 \text{ V/V}$$


$$A_{v_{cm}} = -0.629 \text{ V/V}$$

Output resistance

$$R_o = \frac{I}{g_m} \quad \text{if} \quad \begin{array}{l} \text{ideal current} \\ \text{source} \end{array}$$

$$\begin{aligned} R_o &= r_o \parallel \frac{1}{g_m} \quad \text{if} \quad \begin{array}{l} \text{current source} \\ \text{resistance is} \end{array} \\ &= 20 \parallel \frac{1}{0.6245} \quad r_o \\ &= 1.48 \quad \underline{\text{k}\Omega} \end{aligned}$$

Cascode

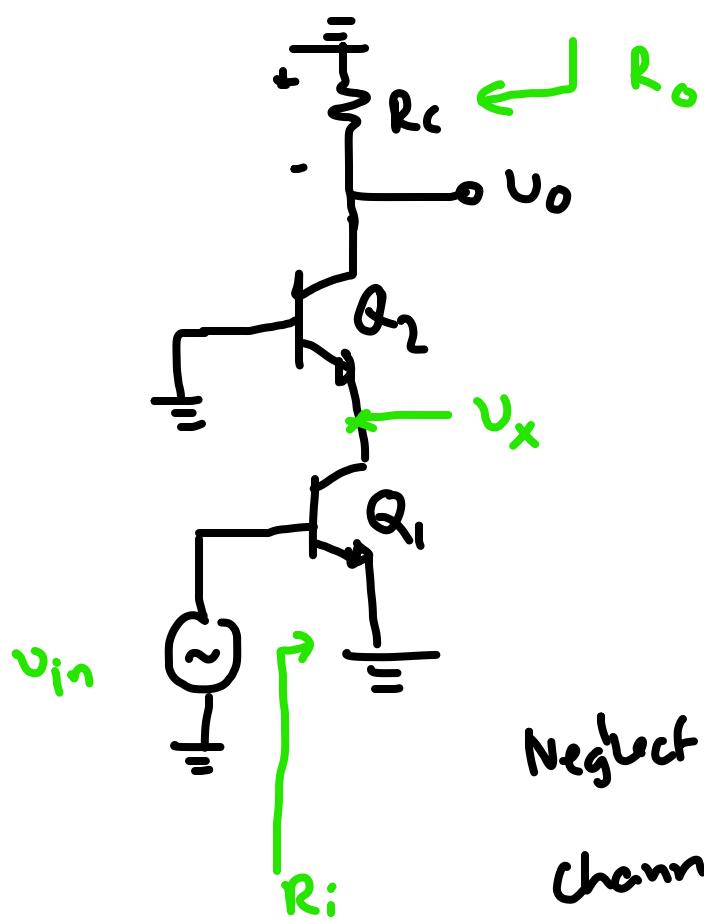

Neglect the
channel length modulation

$$R_i = r_{\pi 1}$$

$$r_{\pi 1} = \frac{\beta}{g_m 1}$$

$$R_o = R_C$$

$$v_o = -i_{C2} R_C$$

$$= -g_{m2} v_{be2} R_C$$

$$= -g_{m2} (v_{be2} - v_{ce2}) R_C$$

$$= -g_{m2} (0 - v_x) R_C = g_{m2} v_x R_C$$

$$\left| \frac{v_x}{v_{in}} = -\underline{g_{m1}(r_{e2})} \right.$$

$$\frac{v_o}{v_n} = g_{m2} R_C$$


$$A_v = - (g_{m1} r_{e2}) g_{m2} R_C$$

$$= - g_{m1} \frac{\alpha_2}{g_{m2}} g_{m2} R_C$$

$$= - \alpha_2 g_{m1} R_C \approx - \beta_{m1} R_C$$

Cascode

MOSFET

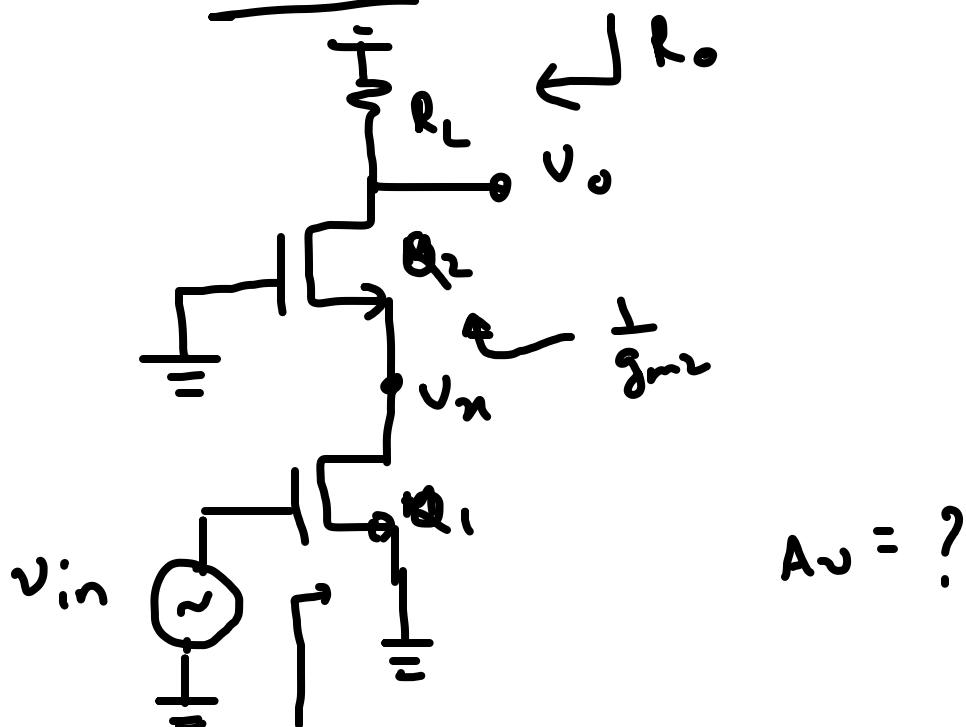

Neglect channel length modulation


$$R_i = \infty$$

$$R_o = \infty$$

$$\frac{v_o}{v_{in}} = g_{m2} R_L$$


$$\frac{v_o}{v_{in}} = - g_{m1} \frac{1}{g_{m2}} = - \frac{g_{m1}}{g_{m2}}$$


$$\frac{v_o}{v_{in}} = - g_{m1} R_L$$

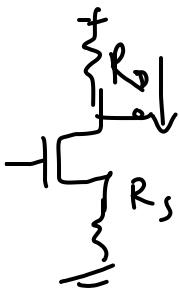

exp v_{in} \rightarrow 15 \rightarrow Multi
 \rightarrow 40 \rightarrow Diff.
 \rightarrow 25 \rightarrow Int + sin
 \rightarrow 10 \rightarrow Coss.
 $\frac{10}{10} \rightarrow$ U

Consider channel length modulation

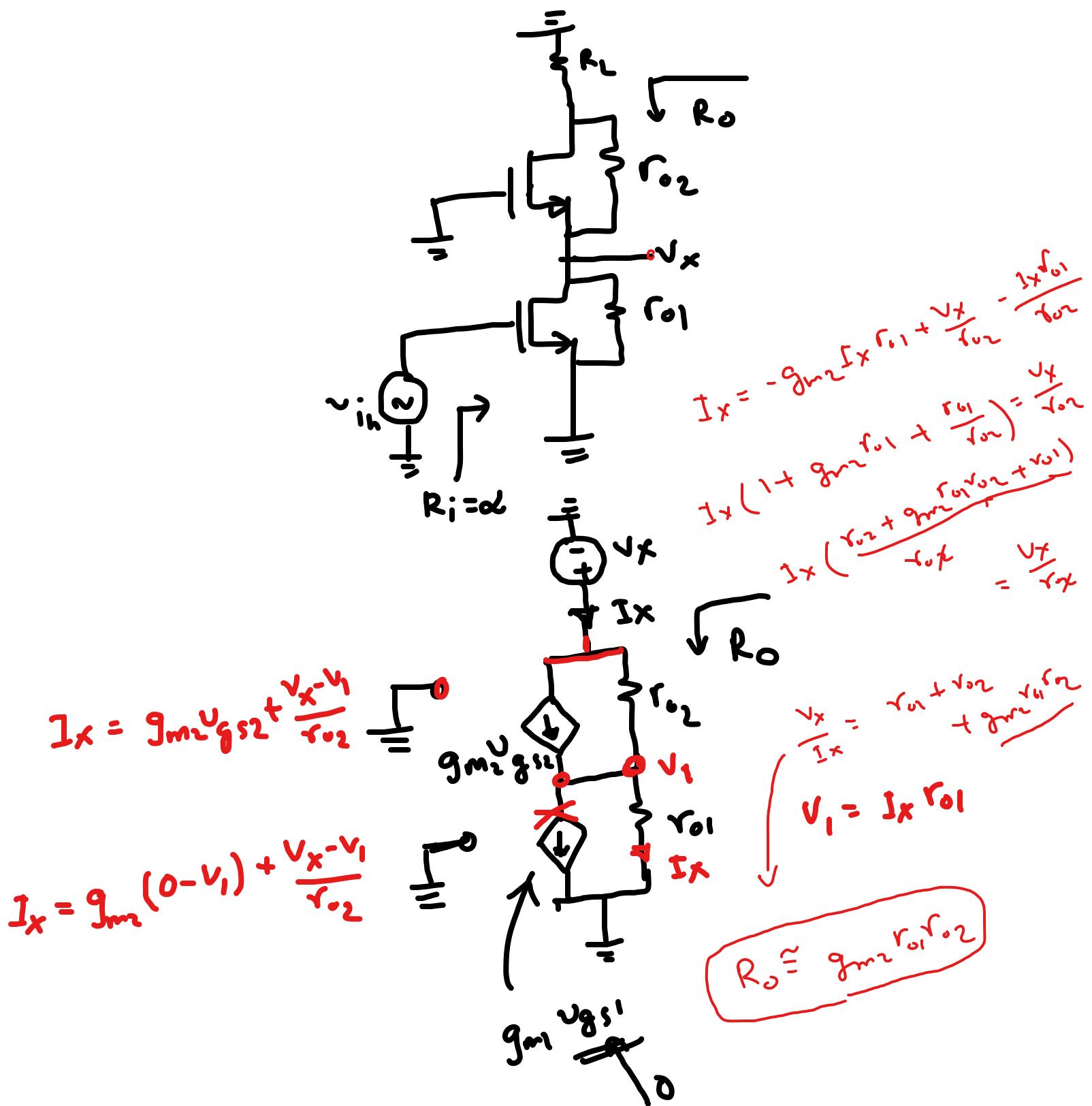

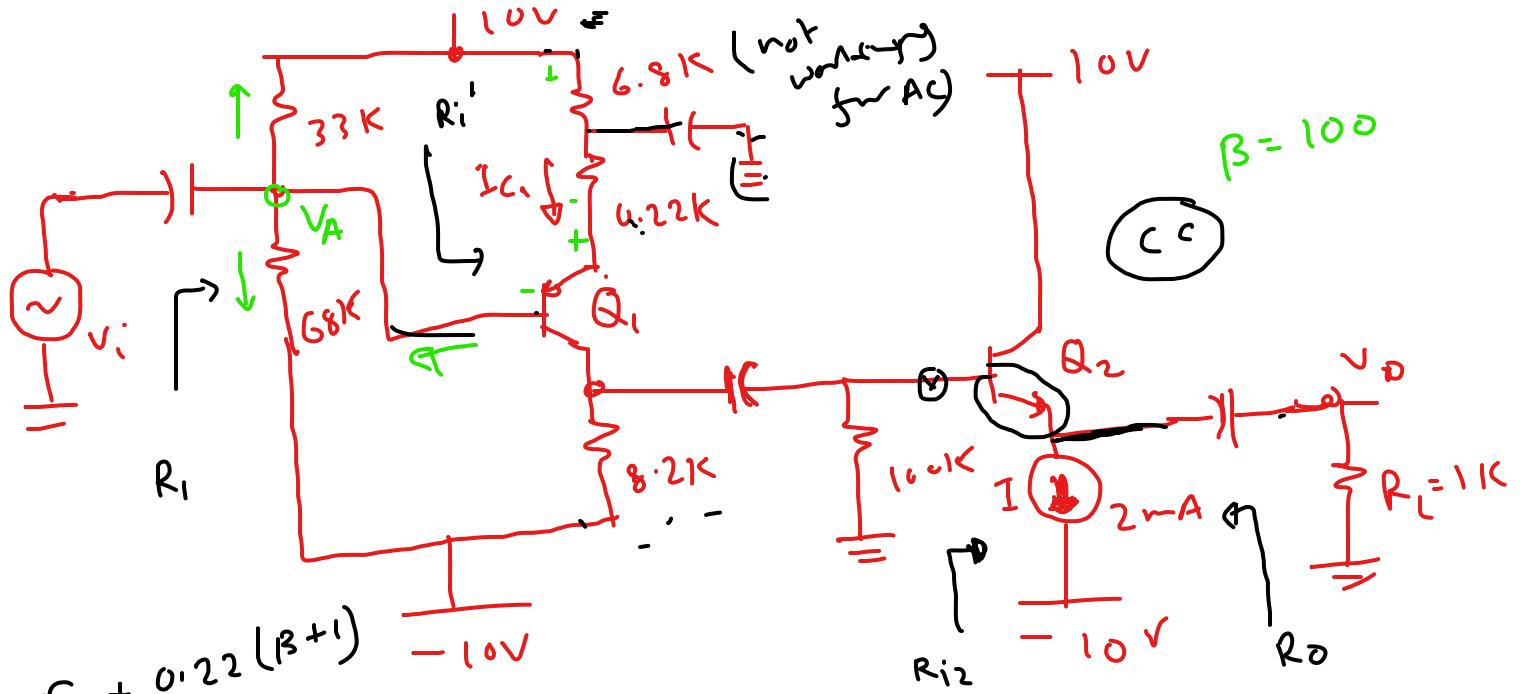

$$R_i^r = r_{\pi 1} + 0.22(\beta + 1)$$

$$R_i = 33 // 6.8 // \frac{V_A - 10}{33} + \frac{V_A + 10}{6.8} - I_B = 0 \quad V_A \left(\frac{1}{33} + \frac{1}{6.8} \right) - I_B = \frac{10}{33} - \frac{10}{6.8}$$

$$10 - (6.8 + 0.22)(\beta + 1) I_B - 0.7 = V_A$$

$$V_A + 709.02 I_B = 9.3 \quad \text{--- (II)}$$

$$R_o = r_{e2} + \frac{100 // 8.2}{(\beta + 1)}$$

$$V_A = 3.64 \text{ V}$$

$$I_B = 7.98 \text{ mA}$$

$$I_C = 100 \times 7.98 \text{ mA} = 0.798 \text{ mA}$$

$$R_{i2} = r_{\pi 2} + \frac{R_L(\beta + 1)}{R_L(\beta + 1)}$$

$$g_{m1} = 40 I_C$$

$$\gamma_{\pi 1} = \frac{\beta}{g_{m1}}$$

$$A_{v1} = A_{v1} A_{v2}$$

$$A_{v1} = - \frac{g_{m1} (8.2 // 100 // R_{i2})}{1 + g_{m1} (0.22)}$$

$$A_{v2} = \frac{R_L}{r_{e2} + R_L}$$

$$I_{C2} = I_{e2} \times \frac{\beta}{(\beta + 1)} = 2 \times \frac{100}{101}$$

$$g_{m2} = 40 I_{C2} \quad r_{\pi 2} = \frac{\beta}{g_{m2}}$$