
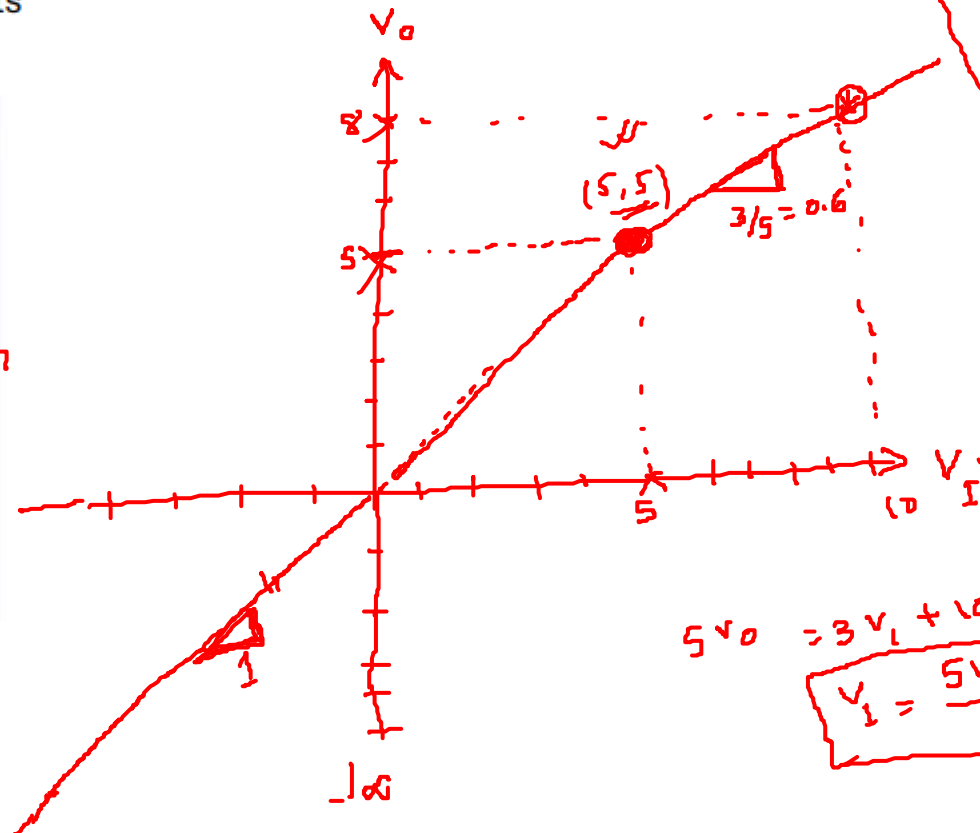


Q1. Consider a wave shaping circuit powered by a supply voltage $V_{cc} = 4.3\text{ V}$ and assume that each diode in the circuit has a constant forward voltage drop of $V_D = 0.7\text{ V}$.

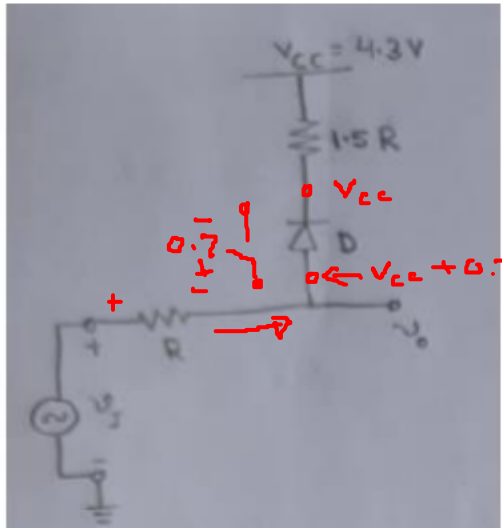Task:

Ideal

- Derive the mathematical expression for the transfer characteristics, i.e., the relationship between the input voltage V_I and the output voltage V_O .
- Plot the transfer curve (V_I vs. V_O), clearly indicating:
 - The slopes of each segment
 - The coordinates of all breakpoints



If D is OFF $V_O < V_{cc} + 0.7$
 $V_O < 4.3 + 0.7$
 $V_O < 5\text{ V}$

If D is ON $V_O > 5$

KVL:

$$+V_I - IR - 0.7 - 1.5R = 4.3$$

$$V_I - 5 = 2.5IR$$

$$I = \frac{V_I - 5}{2.5R}$$

$$V_O = V_I - IR = V_I - \frac{V_I - 5}{2.5R} R$$

$$= \frac{2.5V_I - V_I + 5}{2.5}$$

$$= \frac{1.5V_I}{2.5} + 2$$


$$5V_O = 3V_I + 10$$

$$V_I = \frac{5V_O - 10}{3}$$

$$V_O = \frac{3}{5}V_I + 2$$

say, $V_I = 10\text{ V}$
 $V_O = 8$

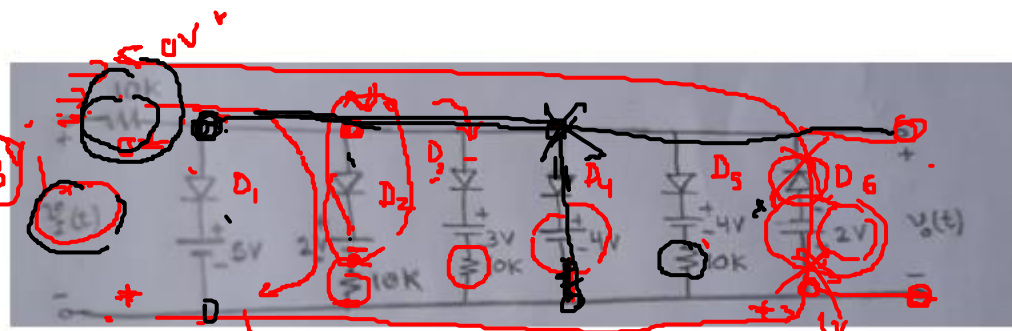Q2. Plot the transfer characteristics of the following circuit. Assume all diodes are ideal.



$V_i \rightarrow -\infty$ to $+\infty$

At negative V_i , $D_1 \sim D_5$ are OFF

D_6 ON — $V_i > 2V$ — $V_o = -2V$

OFF $\rightarrow V_i < 2V$ $V_o = V_i$
negative

$D_2 + D_3 \rightarrow$ ON

$$\frac{V_i - V_o}{10} = \frac{V_o - 2}{10} + \frac{V_o - 3}{10}$$

$V_i > 4V$
 D_4 ON
 $V_o = 4V$

$V_i \rightarrow$ Positive
 $V_i > 2$, $D_2 \rightarrow$ ON $D_1, D_3 - D_6$ OFF


$$\frac{V_i - V_o}{10} = \frac{V_o - 2}{10}$$

$$V_i - V_o = V_o - 2$$

$$2V_o = V_i + 2$$

$$V_o = \frac{V_i}{2} + 1$$

(a) $V_i > 3$

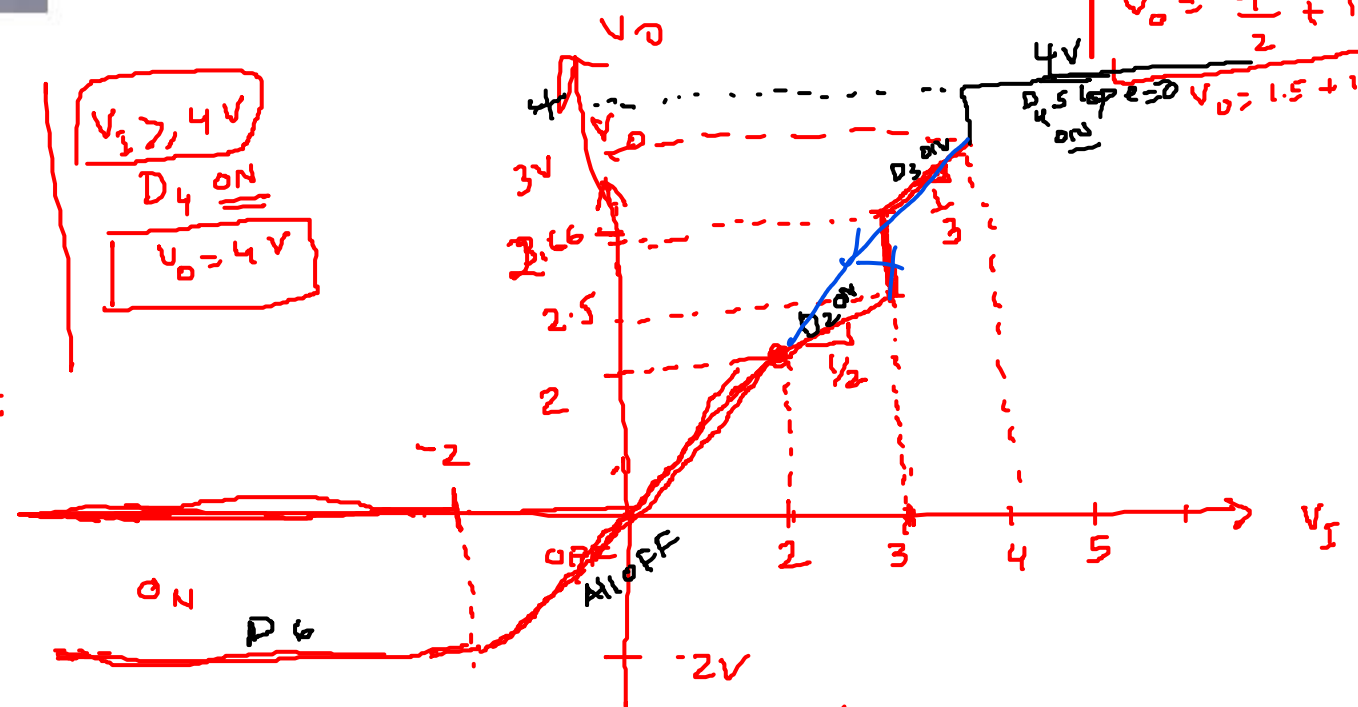


$$V_i - V_o = V_o - 2 + V_o - 3$$

$$V_i = 3V_o - 5$$

$$V_o = \frac{V_i}{3} + \frac{5}{3}$$


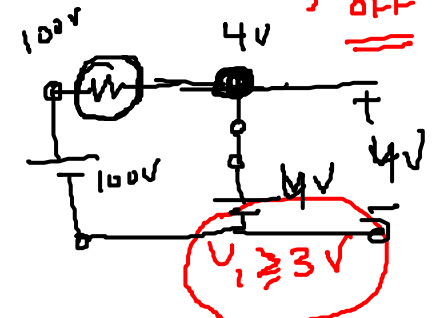
$V_i > 3$, $V_o = 3.66$
 $V_i = 4$, $V_o = 3$



Sorry, I found a mistake here.

please see the solution posted on d2L

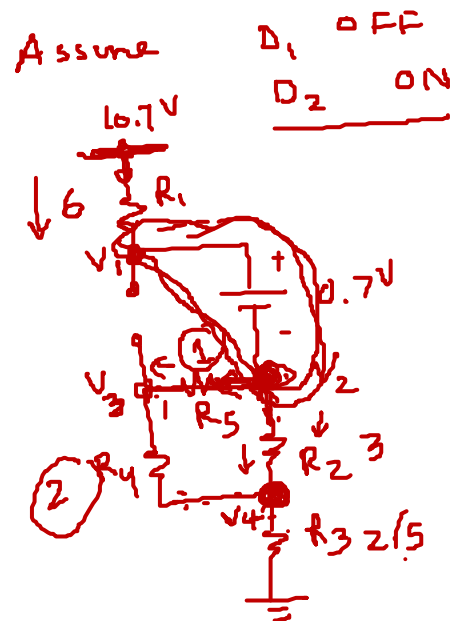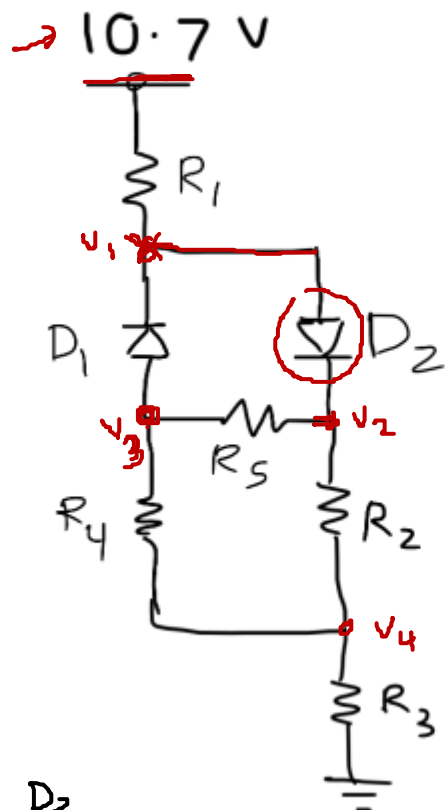Q3. In the diode circuit of the following figure, D_1 and D_2 are silicon diodes with on-state voltage drop may be assumed constant at 0.7V. If $R_1 = 6k\Omega$, $R_2 = 3k\Omega$, $R_3 = 2.5k\Omega$, $R_4 = 2k\Omega$ and $R_5 = 1k\Omega$, determine all node voltage.



$$R_T = (R_5 + R_4) \parallel R_2 + R_3 + R_1$$

$$= (1 + 2) \parallel 3 + 2.5 + 6$$

$$= 1.5 + 2.5 + 6 = 10 \text{ V}$$

$$I = \frac{10.7 - 0.7}{10} = 1 \text{ mA}$$

$$V_1 = 10.7 - 6 \times 1 = 10.7 - 6 = 4.7 \text{ V}$$

$$V_2 = V_1 - 0.7 = 4.7 - 0.7 = 4 \text{ V}$$

$$V_4 = 2.5 \times 1 = 2.5 \text{ V}$$

$$I_{R_2} = \frac{V_2 - V_4}{R_2} = \frac{4 - 2.5}{3} = \frac{1.5}{3} = 0.5 \text{ mA}$$

$$V_3 = V_2 - 1 \times 0.5 = 4 - 0.5 = 3.5 \text{ V}$$

D_1	D_2
OFF	OFF
ON	OFF
OFF	ON
ON	ON

D_2 ON

$$10.7 > V_1 > V_2 > V_3 > V_4$$



D_1 OFF

$$\frac{10.7 - V_1}{6} = \frac{V_1 - 0.7 - V_4}{3} + \frac{V_1 - 0.7 - V_3}{1}$$

$$\frac{V_2 - V_4}{3} + \frac{V_3 - V_4}{2} = \frac{V_4}{2.5}$$

$$V_2 = V_1 - 0.7$$

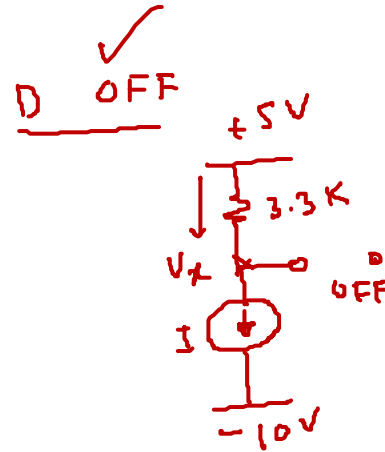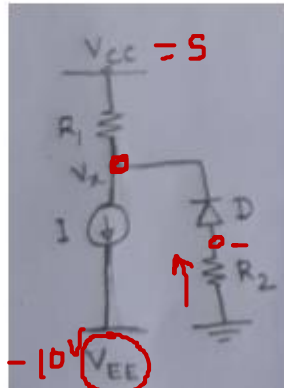Q4. In the following circuit, D is a silicon diode with on-state voltage drop $V_D = 0.7V$. If $V_{CC} = 5V$, $V_{EE} = -10V$, $R_1 = 3.3\text{ k}\Omega$, $R_2 = 2.2\text{ k}\Omega$ and $I = 4.0\text{ mA}$, determine V_x .



$$5V_x = -18.5V$$

$$V_x = \frac{-18.5}{5} = -3.7V$$

$$I_{2.2} = \frac{-3.7 + 0.7}{2.2} = \frac{-3}{2.2}$$

$$= -1.36\text{ mA}$$

$$V_1 = 1.36 \times 2.2 = 3V$$

$$V_x = 5 - 3.3I$$

$$= 5 - 3.3 \times 4$$

$$= 5 - 13.2 = -8.2V$$

$$V_D = 0 - (-8.2) = 8.2 > 0.7V$$

(inconsistent)

$$V_D = 3 - (-3.7)$$


$$= 6.7V$$

0.7V Consistent

$$\frac{V_x - 5}{3} + \frac{V_x + 0.7}{2} + 4.4 = 0$$

$$2V_x - 10 + 3V_x + 2.1 + 26.4 = 0$$

Optional work

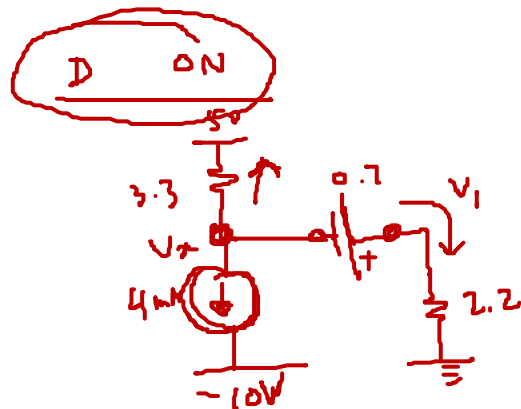


Nodal equation

$$\frac{V_x - 5}{3.3} + \frac{V_x + 0.7}{2.2} + 4 = 0$$

Q5.


Assuming $V_{D_{cutt-in}} = 2.2\text{ V}$ and $V_D = 2.5\text{ V}$, find states of D_1 and D_2 . Also calculate V . If

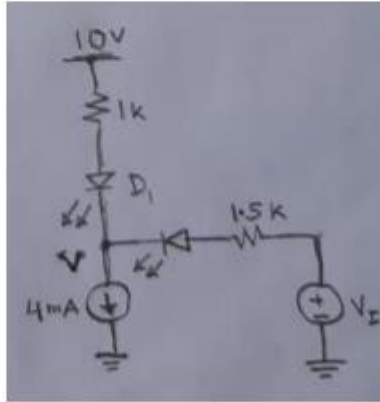- a. $V_{in} = 0\text{ V}$, and
- b. $V_{in} = 16.5\text{ V}$




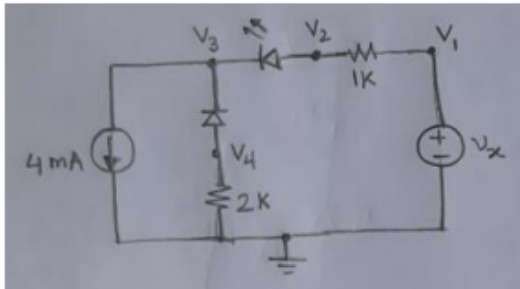Q6. $V_{D1}=0.7\text{ V}$ and the LED D_2 starts to glow at 2.2V forward voltage. Find V_1 , V_2 , V_3 , V_4

- if V_x is so negative that LED is dark.
- If V_x is gradually increased until D_2 starts to glow.



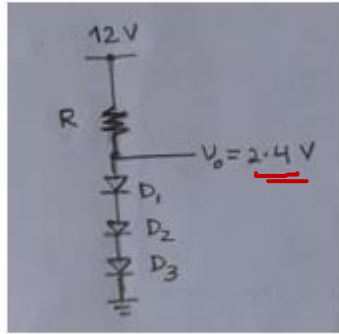Q7. In the following circuit, diodes exhibit a forward voltage drop of 0.65V at 0.1mA. Determine R and power consumption in R such that $V_o = 2.4V$.



exponential diode model

$$V_o = 2.4$$

$$V_D = \frac{2.4}{3} = 0.8V$$

$$I_D = I_S e^{V_D / V_T}$$


$$\frac{I}{0.1} = e^{\frac{V_{D2} - V_{D1}}{V_T}} = e^{\frac{0.8 - 0.65}{0.025}}$$

$$I = \cancel{0.1} \times 40.34 \text{ mA}$$

$$R = \frac{12 - 2.4}{40.34} = 238 \underline{\underline{\Omega}}$$


$$V_T = 25 \text{ mV}$$
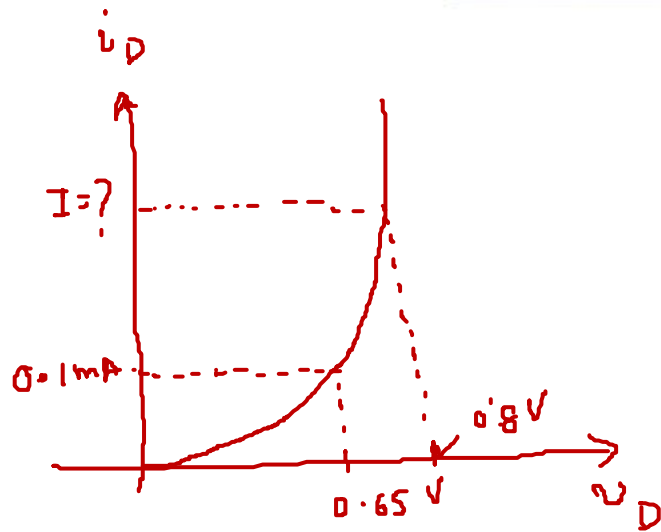
$$\begin{aligned} P &= I^2 R \\ &= (40.34)^2 \times 238 \\ &= 0.387 \underline{\underline{W}} \end{aligned}$$



Temperature dependence circuits

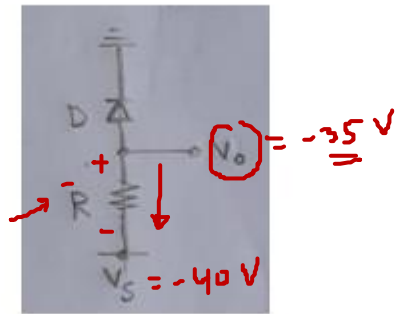Q1. In the circuit below, $V_s = -40\text{ V}$ and D is a typical silicon diode. If $V_o = -35\text{ V}$ at an ambient temperature of 30°C , determine V_o at 50°C . Assume that the reverse current of the diode does not depend upon the voltage across the diode and that the diode does not enter its breakdown region.



30°C

$$V_o = -40 + 20 \\ = -20\text{ V}$$

Current doubles every


$$i_{D2} = 4 i_{D1}$$

10°C


increase in temperature at RB condition.

$$i_{D1} R = -35 - (-40) = 5\text{ V} \quad @ \quad 30^\circ\text{C}$$

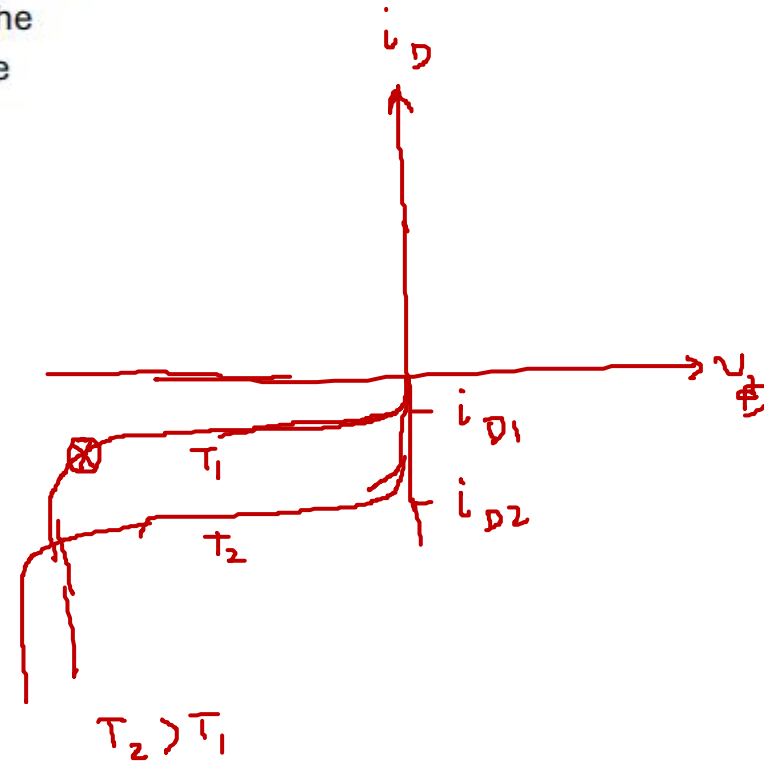
$$\text{at } 50^\circ\text{C} \quad V_R = i_{D2} R = 4 i_{D1} R = 20\text{ V}$$



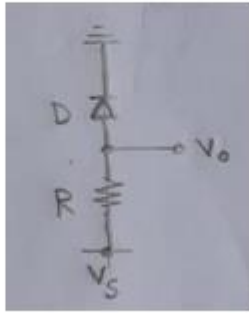
Q2. In the following circuit, $V_s = -20\text{ V}$, $V_o = -12\text{ V}$ at 20°C , find V_o at 40°C and 0°C temperature. Assume, the diode is not in reverse breakdown.



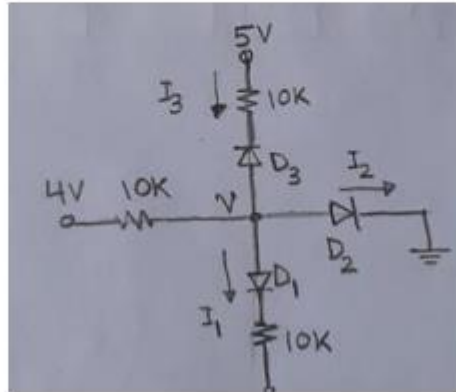Q4. In the circuit shown below, the diodes have a constant forward voltage drop $V_D = 0.7\text{ V}$. Determine the current I_1 , I_2 , I_3 , and V .



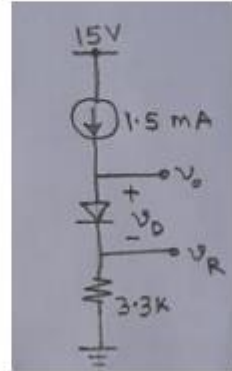
Q3. For the following circuit, find V_D at 40°C , 80°C , and 0°C . At 20°C , $V_o=5.7\text{V}$ and $V_R=4.95\text{V}$.



Rectifier and regulator circuits

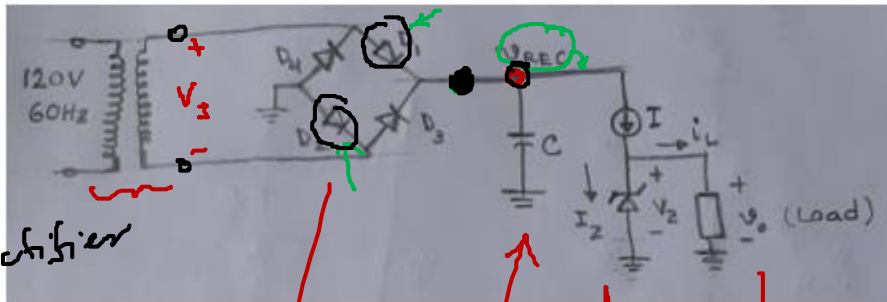Q1. The following figure shows an isolated bridge rectifier feeding a load. The load voltage V_o is regulated by a Zener diode with $I_{zk}=3.0$ mA. The Zener diode is energized by a current source, I , and the load current i_L can be variable, but it does not depend on the load voltage. Diodes exhibit an on-state voltage drop 0.7V, $C=100\mu\text{F}$, $V_{rec}=20\text{V}$ and $V_r=4\text{V}$.

- Determine the rms value of the secondary transformer (120: 15) voltage V_1 , the reading of a DC voltmeter of V_{rec} , and the maximum current that the load is permitted to draw if this circuit is to function properly.
- Determine V_{zo} and r_z of the Zener diode if the regulated voltage is desired to be 10V for a load current of 25mA. The load voltage variation is to be 160mV when the load current varies from zero to 40mA. Finally, for a load current of 25mA, draw the waveform of the load voltage v_o .



DC o/p of rectifier

$$\frac{2\hat{V}}{\pi} = \frac{2 \times 20}{\pi}$$

$$= 12.73$$

↑ before the capacitor

Rectifier

Filter

Regulator

Reading of DC voltmeter


$$V_{DC} = 18\text{V} = \overline{V_{rec}}$$

↑ after capacitor

\hat{V} = peak voltage

\hat{V}_r = minimum voltage

\overline{V} = average voltage

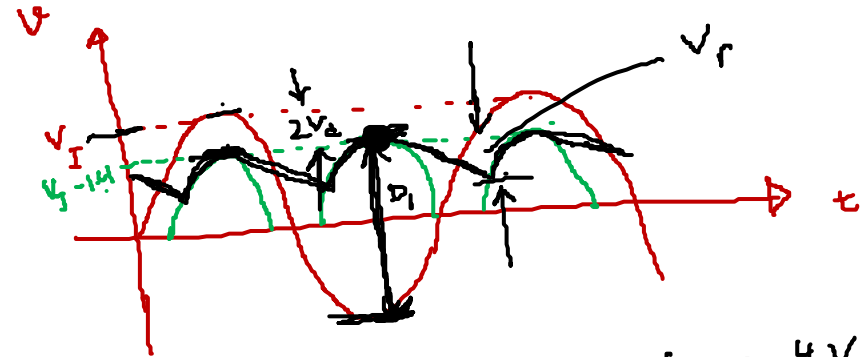


$$\hat{V}_{rec} = 20\text{V}, \quad V_r = 4\text{V}$$

$$\text{minimum } V_{rec} = 20 - 4 = 16\text{V}$$

$$\overline{V}_{rec} = \frac{20 + 16}{2} = 18\text{V}$$

$$V_1 = 20 + 1.4 = 21.4\text{V}$$
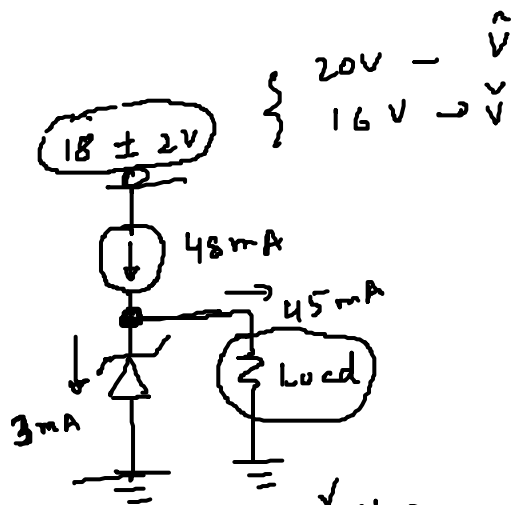
$$V_{1,rms} = \frac{21.4}{\sqrt{2}} = 15.13\text{V}$$



$$V_r = \frac{I}{2fC}$$


$$4 = \frac{I}{2 \times 60 \times 100 \times 10^{-6}}$$

$$I = 0.048 = 48 \text{ mA}$$

$$I_{L-\max} = 48 - \underline{I_{ZK}}$$

$$= 48 - 3 = 45 \text{ mA}$$
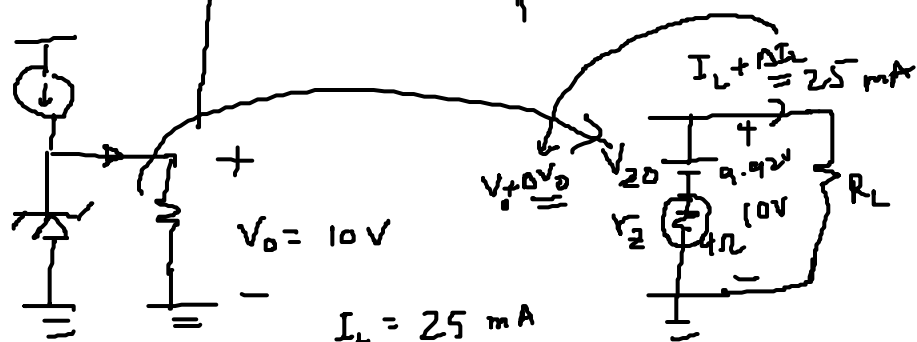
$$R_{L-\min} = \frac{10}{45 \text{ mA}} = 222 \Omega$$



$$V_Z = V_{Z0} + (I_Z - \underline{I_{ZK}}) r_Z$$


$$I_Z = 48 - 25 = 23 \text{ mA}$$

$$10 = V_{Z0} + (23 - 3) r_Z$$

$$V_{Z0} = 10 - 20 \times 4 \times 10^{-3} = 9.92 \text{ V}$$



$$r_Z = \frac{\Delta V_0}{\Delta I_L} = \frac{160}{40} = 4 \Omega$$
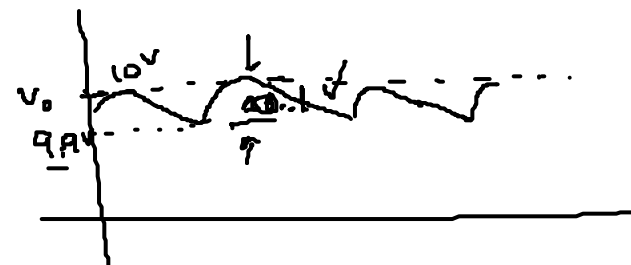
$$\Delta V_0 = \Delta I_L r_Z = 25 \times 4 \text{ mV} = 100 \text{ mV} = 0.1 \text{ V}$$



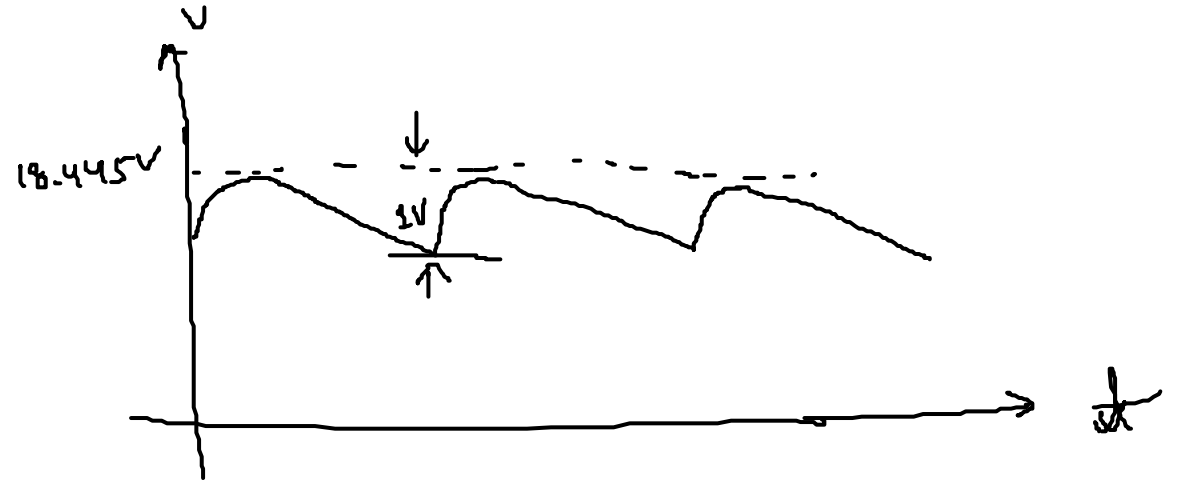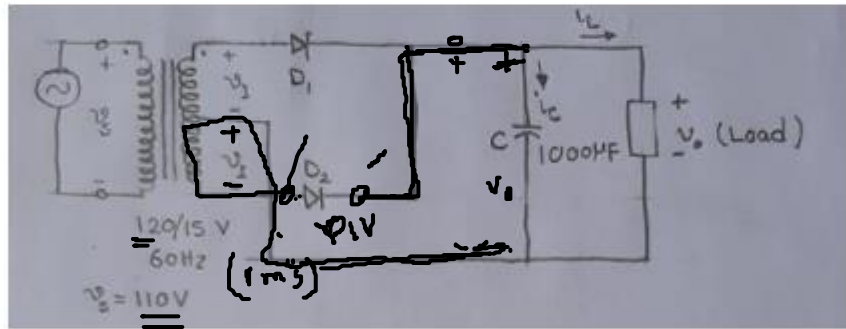Q2. In the following full-wave rectifier circuit, the forward voltage of diode is $V_D = 1 \text{ V}$.

- If $i_L = 120 \text{ mA}$, find \bar{v}_o and V_r .
- If $R_L = 82 \Omega$, find v_o and V_r .
- Calculate PIV using the results obtained in part (b).



$$\text{PIV} - V_o - V_i = 0 \quad \text{PIV} = V_o + V_i$$

$$= 18.445 + 19.445$$

$$= 37.89 \text{ V}$$

$$V_i = \frac{10 \times 15}{120} = 12.5 \text{ V (rms)} \quad V_{I(\text{peak})} = \hat{V}_i = 12.5 \sqrt{2} = 17.68 \text{ V}$$

$$\hat{V}_o = 17.68 - 1 = 16.68 \text{ V}$$

$$\hat{V}_o = 19.445 - 1 = 18.445 \text{ V}$$

$$\hat{V}_o = 17.445 \text{ V}$$

$$\bar{V}_o = 17.445 \text{ V}$$


(b)

$$V_r = \frac{\hat{V}_o}{2fR_L C}$$

$$V_r = \frac{V_L}{2fC} = \frac{120 \text{ mA}}{2 \times 60 \times 1000 \mu\text{F}}$$

$$= \frac{18.445}{2 \times 60 \times 82 \times 1000 \times 10^{-6}} = 1.88 \text{ V}$$
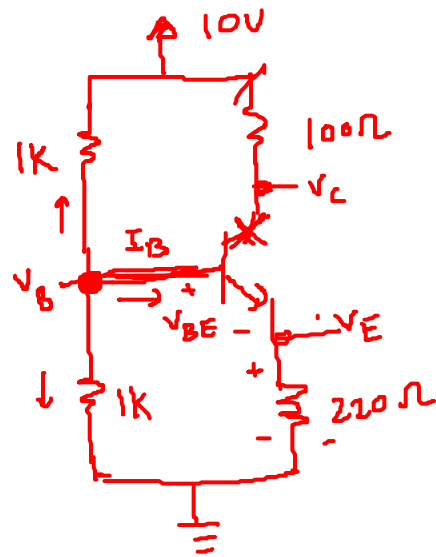
$$\bar{V}_o = 18.445 - \frac{1.88}{2} = 17.50 \text{ V}$$



$$\beta = 100$$

$$V_{BE} = 0.7 \text{ V}$$

KCL :

$$\frac{V_B - 10}{1 \text{ k}} + \frac{V_B - 0}{1 \text{ k}} + I_B = 0$$

$$V_B - 10 + V_B + I_B = 0$$

$$2V_B + I_B = 10 \quad \text{--- (i)}$$

$$V_B - 0.7 - 0.220 I_E = 0$$

$$V_B - 0.22(\beta + 1)I_B = 0.7$$

$$V_B - 22.22 I_B = 0.7 \quad \text{--- (ii)}$$

$$V_{CE} = V_C - V_E$$

$$= 8.11 - 4.12 = \underline{\underline{3.99}} > V_{CE, \text{sat}} \quad (0.7 \text{ V})$$

BJT is in Active mode

$$V_E = 0.22 \times (\beta + 1) I_B$$

$$= 0.22 \times 101 \times 0.189$$

$$= 4.12 \text{ V}$$

$$V_B = 4.9 \text{ V}$$


$$I_B = 0.189 \text{ mA}$$

$$V_C = 10 - I_C R_C = 10 - \beta I_B \times 0.1$$

$$= 10 - 100 \times 0.189 \times 0.1$$

$$= 8.11 \text{ V}$$
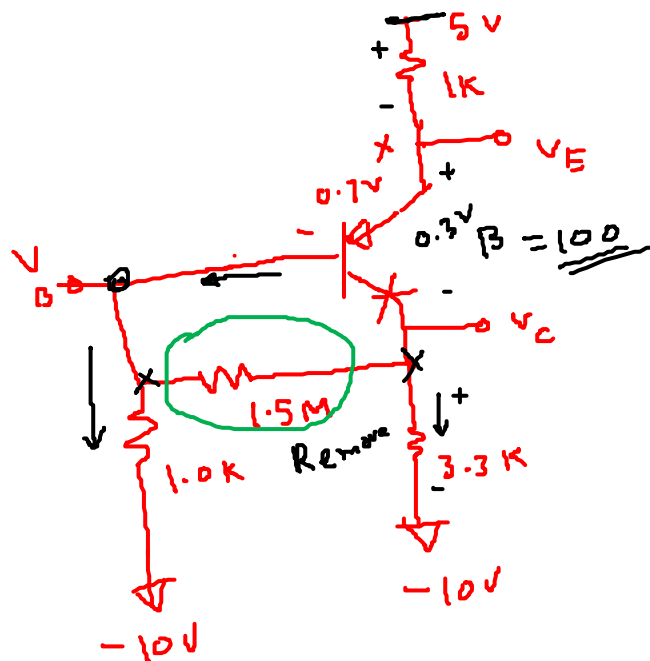
$$\beta_{forced} = \frac{I_C}{I_B} = \frac{1.98}{6.15}$$



BJT in saturation mode

$$5 - I_E(1) - 0.3 - I_C \times 3.3 = -10$$

$$5 - I_E(1) - 0.7 = V_B$$

$$V_B = -10 + I_B(1)$$

$$I_E = I_C + I_B$$

$$-I_E - 3.3 I_C = -14.7$$

$$-I_E - I_B = -14.3$$

$$I_E - I_B - I_C = 0$$

$$I_B = \frac{V_B - (-10)}{1.0}$$

$$V_B + 10 = I_B$$

$$V_B - I_B = -10 \quad \text{--- (1)}$$

$$I_B = 6.15 \text{ mA}$$

$$I_E = 8.14 \text{ mA}$$

$$I_C = 1.98 \text{ mA}$$

$$5 - 1 I_E - 0.7 = V_B$$

$$V_B + (\beta + 1) I_B = 4.3$$

$$V_B + 10 I_B = 4.3 \quad \text{--- (1)}$$






$$V_B = -9.86 \text{ V} = -9.86 \text{ V}$$

$$I_B = \frac{4.3 - (-9.86)}{10} = 0.1402 \text{ mA}$$

$$V_E = 5 - 1 \times 101 \times 0.1402 = -9.16 \text{ V}$$

$$V_C = -10 + \beta I_B \times 3.3 = 36.26$$

$$V_{EC} = -9.86 - 36.26 < V_{EC,sat}$$

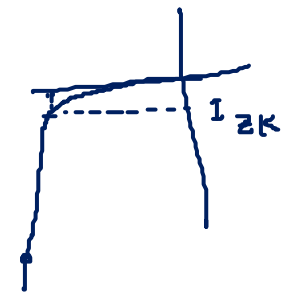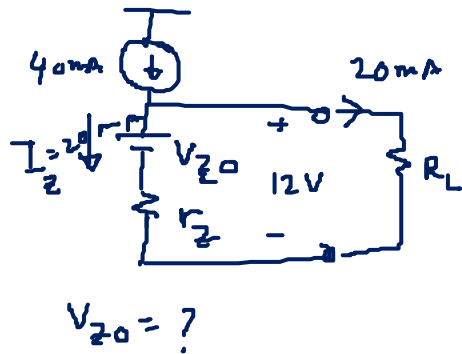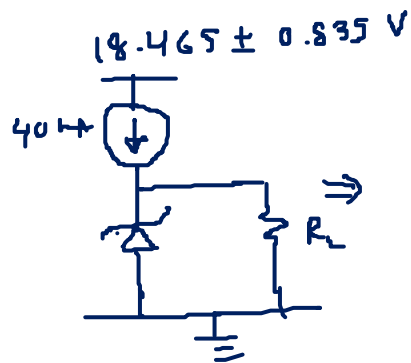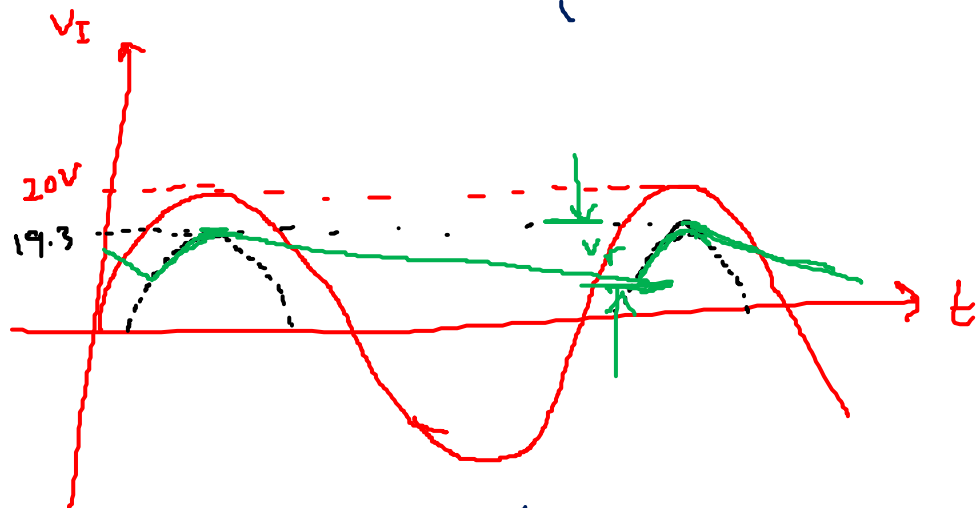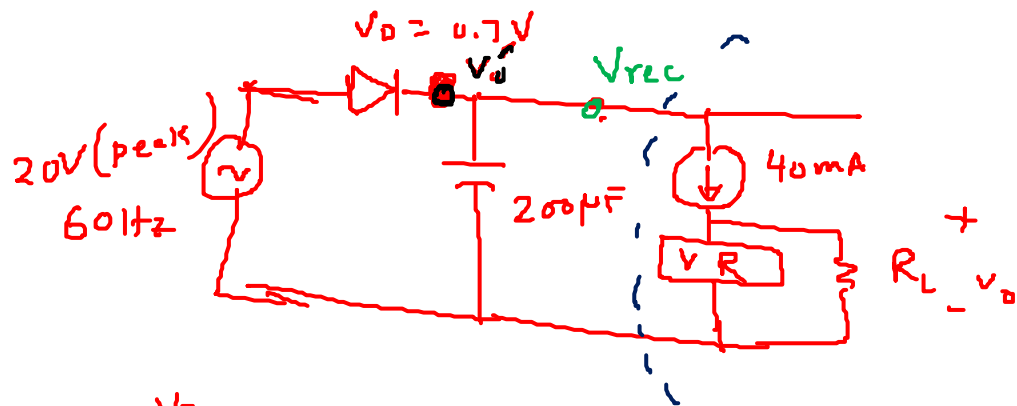

$$20 - 0.7 = 19.3 V$$

$$\hat{V}_o' = 19.3 V$$

$$V_o'_{dc} = \frac{\hat{V}_o'}{\pi} = \frac{19.3}{\pi} = 6.14 V$$

$$\hat{V}_{rec} = \hat{V}_o' = 19.3 V$$

$$V_{rec} = 19.3 - 1.67 = 17.63 V$$

$$\bar{V}_{rec} = \hat{V}_o' - \frac{V_r}{2} = \frac{19.3 + 17.63}{2} = 18.465 V$$

$$V_z = V_{z0} + (I_z - I_{zk}) r_z \quad r_z = 2 \Omega$$


$$12 = V_{z0} + (20 - 2) \times 2 \times 10^{-3} = 11.964 V$$

Another mistake
 $V_r = \frac{1}{fC}$

(before capacitor)

$$V_r = \frac{I}{2fC} = \frac{40 \times 10^{-3}}{2 \times 60 \times 200 \times 10^{-6}} = 1.67 V$$


see midterm solution.

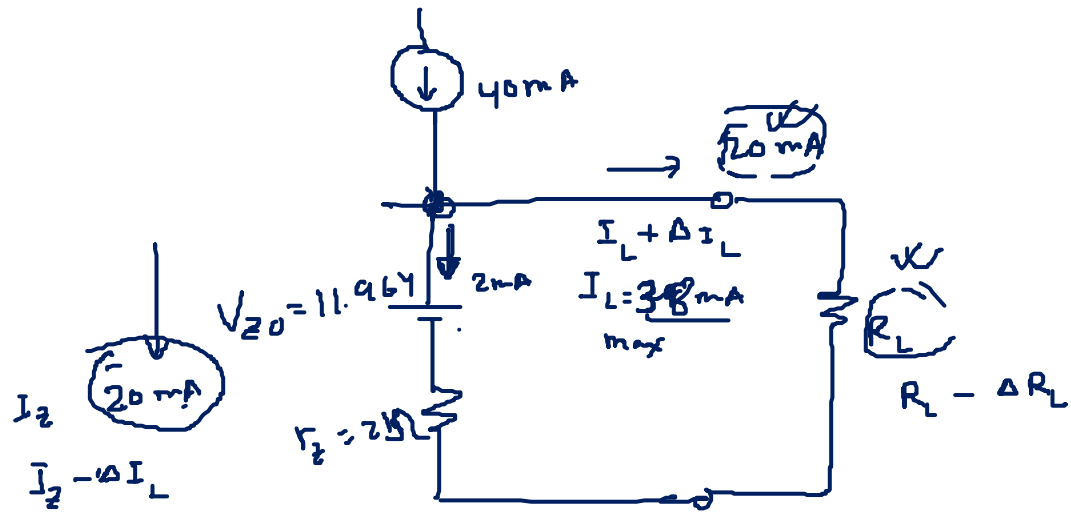

$$R_{L, \min}$$

$$R_{L, \min} = \frac{12}{38\text{mA}} = 316\Omega$$
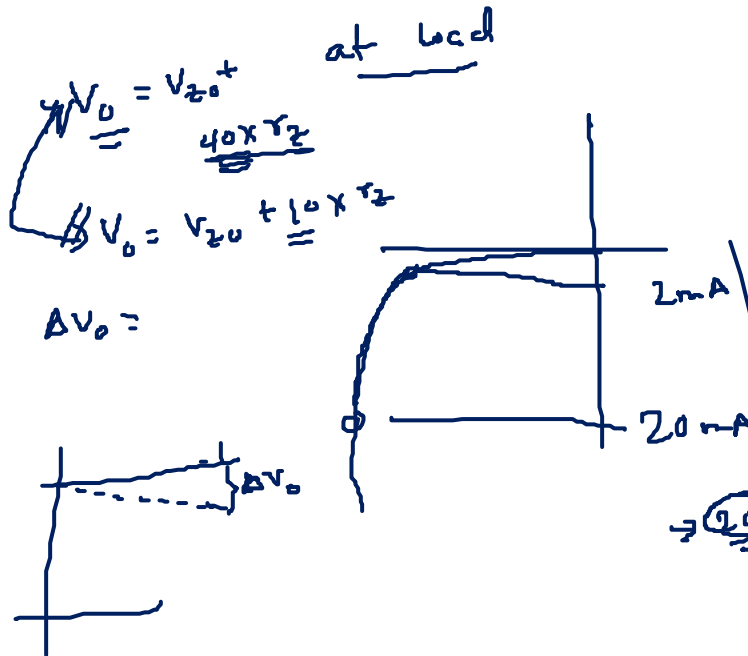
$$\text{Rated Load} = \frac{12}{20\text{mA}} = 0.6\text{K}\Omega$$



$$\Delta I_L = 30\text{mA}$$

$$-\Delta V_o = -\Delta I_L \times r_z = -30 \times 2 = -60\text{mV}$$

$$\% \text{ Voltage regulation} = \frac{60 \times 10^{-3}}{12} \times 100 = 0.5\%$$

