

PRACTICE EXAM

Difficulty: MEDIUM

Questions: 10

Introduction to Circuits Exam

Multiple Choice Questions (4 points each)

Instructions: Choose the best answer for each question.

Question 1: What is the main purpose of the lab described in the document?

- A) To design a new type of circuit.
- B) To introduce the concept of digital logic gates.
- C) To reintroduce circuit concepts like the superposition principle.
- D) To analyze the properties of semiconductors.

Question 2: According to the document, which instruments were used in the lab experiment?

- A) Voltmeter, Ammeter, Ohmmeter
- B) Signal generator, Oscilloscope, Power supply
- C) Logic analyzer, Spectrum analyzer, Function generator
- D) Multimeter, Breadboard, Soldering iron

Question 3: Based on the text, what frequency was supplied by the signal generator during the experiment when creating Table E1?

- A) 1 kHz
- B) 10 kHz
- C) 20 kHz
- D) 50 kHz

Question 4: In the circuit under test, what is the function of the capacitor in Figure 1?

- A) To act as a short circuit.
- B) To act as an open circuit.
- C) To block DC signals.
- D) To amplify AC signals.

Short Answer Questions (8 points each)

Instructions: Answer each question in 2-3 sentences.

Question 5: Explain the objective of the lab in determining the combined RMS output voltage value.

Question 6: State the superposition principle in your own words and explain its relevance to the experimental results.

Question 7: Describe a possible source of error that could account for discrepancies between simulated and experimental results, based on the text.

Problem-Solving Questions (12 points each)

Instructions: Provide detailed explanations for each answer.

Question 8: Based on the information in the tables, calculate the percent difference between the v_O (rms) value in Table E1 and Table E3. Show your work.

Question 9: Describe how the circuit in Figure 1 is simplified for analysis when the capacitor is considered an open circuit (Figures 2a and 2b). What components are analyzed separately?

Question 10: Based on the description of C3, explain the purpose of simulating the circuit in Multisim. What specific elements of the simulated and experimental results are compared and why?